

VLSI Assignment

In this assignment, you will design the hardware to implement the following function:

$$E = A / 2^i + B \times 2^j$$

$$F = E \times C$$

Where:

- A, B, C and E are 8-bit unsigned numbers
- i and j are 3-bit unsigned numbers.
- F is 16-bit unsigned number

Design Specification:

- Implement the design using Verilog language. Do not use the following math operations: -, +, ×, /, shift/rotate. You need to implement them yourself.
- The top design name is mydesign and the port definition is illustrated below. You must use the below testbench and template in your design.
- Use your own choice of multiplier algorithm to implement the multiplier.

Team and Report Rules:

- Teams: you must form a team of 2-3 students.
- Submission and DEMO:
 - What you should submit:
 - Code (Verilog files)
 - Report: which includes
 - the names of the students,
 - status of the code,
 - waveforms.
 - Submission deadline is: 8:00AM on Tuesday 26/12
 - DEMO:
 - Time: during the class of Tuesday 26/12 (9:30-10:30)
 - You will be assigned a time slot to show in the lab
 - You will be asked to explain and modify your code
- This assignment accounts for 15% of your grade. Cheating results in 0-grade.

The followings are the design template and testbench files.

mydesign.v	mydesign_tb.v
<pre> module mydesign (input [7:0] A, input [7:0] B, input [7:0] C, input [2:0] i, input [2:0] j, output reg [15:0] F); /// Your Design endmodule </pre>	<pre> `timescale 1ns/100ps module mydesign_tb; reg [7:0] A; reg [7:0] B; reg [7:0] C; reg [2:0] i, j; wire [15:0] F; // Mydesign one round in hardware mydesign mydesign (.A (A), .B (B), .C (C), .i (i), .j (j), .F (F)); initial begin \$monitor (" (values are in HEX) A=%h B=%h C=%h i=%h j=%h F=%h", A, B, C, i, j, F); A= 8'h06; B=8'h06; C=8'h06 ; i=3'h1; j=3'h1; #10; A= 8'h01; B=8'h01; C=8'h01 ; i=3'h1; j=3'h1; #10; A= 8'hFF; B=8'hFF; C=8'hFF ; i=3'h7; j=3'h7; #10; A= 8'hFF; B=8'hFF; C=8'hFF ; i=3'h0; j=3'h0; #10; \$stop; end endmodule </pre>

Correct Output

```

# (values are in HEX) A=06 B=06 C=06 i=1 j=1 F=005a
# (values are in HEX) A=01 B=01 C=01 i=1 j=1 F=0002
# (values are in HEX) A=ff B=ff C=ff i=7 j=7 F=807f
# (values are in HEX) A=ff B=ff C=ff i=0 j=0 F=fd02

```